

Reg No.: \_\_\_\_\_

Name: \_\_\_\_\_

**APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY**  
THIRD SEMESTER B.TECH DEGREE EXAMINATION, DECEMBER 2018

**Course Code: EC207**

**Course Name: LOGIC CIRCUIT DESIGN (EC, AE)**

Max. Marks: 100

Duration: 3 Hours

**PART A**

*Answer any two full questions, each carries 15 marks.*

Marks

- 1 a) Convert the following (8)
- (i)  $(AB6)_{16}$  to Decimal (iii)  $(543.26)_{10}$  into Octal
- (ii)  $(247.36)_8$  into Hexa Decimal (iv)  $(AF9.B0D)_{16}$  into Binary
- b) Consider the signed binary numbers  $A = 01000110$  and  $B = 11010011$  where B is in 2's complement form. Find the value of the following mathematical expression (7)
- (i)  $A + B$
- (ii)  $A - B$
- (iii)  $B - A$
- 2 a) Hamming code was used to generate parity for a nibble. If received bit sequence is 0101010 then write correct bit sequence with (i) Even parity (ii) Odd parity (8)
- b) Explain the operation of a 8x1 multiplexer and implement the following using an 8x1 multiplexer (7)
- $F(A, B, C, D) = \sum m(0, 1, 3, 5, 6, 7, 8, 9, 11, 13, 14)$
- 3 a) Minimize the following logic function using K- maps and realize using NAND gates alone (10)
- $F(A, B, C, D) = \sum m(0, 3, 5, 8, 9, 11, 15) + d(2, 3)$
- b) Design a magnitude comparator to compare two 2-bit numbers  $A = A_1A_0$  and  $B = B_1B_0$  (5)

**PART B**

*Answer any two full questions, each carries 15 marks.*


- 4 a) Draw the circuit and explain the operation of TTL NAND gate (10)
- b) Compare TTL, CMOS logic families in terms of fan-in, fan-out, supply voltage, propagation delay, power dissipation and noise margin (5)
- 5 a) Implement the following function using PLA (8)
- $F1(x, y, z) = \sum m(1, 2, 4, 6)$
- $F2(x, y, z) = \sum m(0, 1, 6, 7)$

- b) Explain a MOD 6 asynchronous counter using J K Flip Flop (7)
- 6 a) Design a 3-bit synchronous counter using D Flip Flop (10)
- b) Convert SR Flip Flop into J K Flip Flop (5)
 
### PART C

*Answer any two full questions, each carries 20 marks.*

- 7 a) Draw the logic diagram of 3 bit PIPO shift register with LOAD/SHIFT control and explain its working. (10)
- b) Explain Moore and Mealy machine models. Compare the models (10)
- 8 a) Draw the logic diagram of 3-bit Johnson counter and explain the working with truth table. (10)
- b) For the given state diagram, design a sequential circuit with D flip flops (10)



- (i) Construct the state table.
- (ii) Obtain the simplified input equations for all input flip flops and the simplified equation for the output.
- 9 a) Minimize the state table using implication chart. (10)

Present state	Next state		Output ( $Z_1Z_2$ )	
	X=0	X=1	X=0	X=1
0	0	1	00	00
1	4	2	00	00
2	7	1	00	00
3	2	6	01	10
4	6	5	10	00
5	3	4	01	11
6	1	6	01	10
7	3	8	10	00
8	8	7	01	11

- b) Design a 101 sequence detector ,for overlapping case, using D Flip Flop (10)

\*\*\*\*