
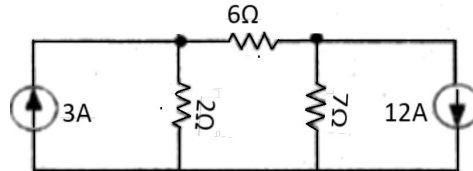


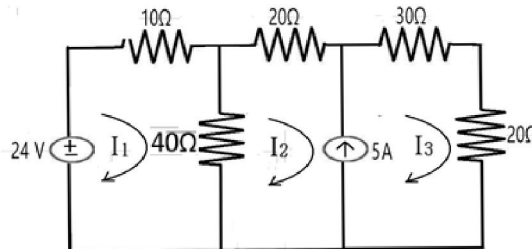
- 13 a) Find the current through the  $6\Omega$  resistor using Nodal Analysis. (4)



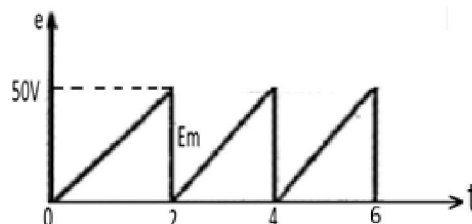- b) Using Mesh Analysis determine the currents  $I_1$ ,  $I_2$  and  $I_3$  in the circuit shown in figure. (6)



- 14 a) A circular iron ring has a cross-sectional area of  $0.01\text{m}^2$  and a mean circumference of  $1.5\text{m}$ . A saw cut of  $4\text{mm}$  wide is made in the ring. Calculate the magnetising current required to produce a flux of  $0.8\text{mWb}$  in the air gap if the ring is wound with a coil of 175 turns. Assume relative permeability of iron as 400 and leakage factor as 1.25. (5)
- b) Define the terms flux, permeability and m.m.f with respect to magnetic circuits. (5)
- 15 a) Find the form factor of the waveform shown in figure. (5)



- b) A coil of resistance  $8\Omega$  and inductance  $0.03\text{H}$  is connected to an a.c supply of  $240\text{V}$ ,  $50\text{Hz}$ . Calculate: (5)
- The current, power and power factor of the circuit.
  - The value of capacitance which when connected in series with the above coil causes no change in the value of current and power taken from the supply.
- 16 A non-inductive resistor of  $10\Omega$  is connected in series with a choke coil having internal resistance of  $1.2\Omega$  and is fed from a  $200\text{V}$ ,  $50\text{Hz}$  supply. Current flowing through the circuit is  $8\text{A}$ . Calculate: (10)
- Inductance of the choke coil
  - Voltage across the choke coil
  - Power absorbed by the choke coil
  - Power absorbed by non-inductive resistor
  - Total power absorbed.
  - Phasor diagram of the voltages in the


circuit.

### PART C

*Answer any one full question from each module, each carries 10 marks.*
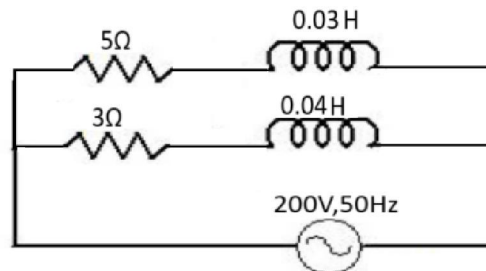
#### Module V

- 17 a) What is active power and reactive power in an ac circuit? Explain. (4)  
 b) For the circuit shown in figure determine: (6)  
 i) The admittance in each branch ii) Total admittance iii) Total current drawn iv) Circuit power factor v) Power absorbed.



- 18 a) Draw the resonance curve of series RLC circuit (3)  
 b) A series RLC circuit has  $R=5\Omega$ ,  $L=0.2\text{H}$  and  $C=50\mu\text{F}$ . The applied voltage is 200V. Find the: (7)  
 i) Resonant frequency ii) Q-factor iii) Band width  
 iv) Half power frequencies v) Current at resonance vi) Current at half power points  
 vii) Voltage across inductance at resonance.

#### Module VI

- 19 a) What are the advantages of three-phase system over single-phase system? (4)  
 b) A balanced delta connected load consists of  $(5+j3)\Omega$  in each branch. The line voltage is  $300\sqrt{2}$  volts. Find: (6)  
 i) Line and phase currents ii) Real and apparent power.  
 20 a) Show that power consumed by three identical single-phase loads connected in delta is equal to three times the power consumed when the loads are connected in star. (6)  
 b) In the two-wattmeter method of 3 phase power measurement, the power input to load is 30kW at 0.397 lagging. Find the reading of each wattmeter. (4)

\*\*\*\*